

KATHMANDU UNIVERSITY
End Semester Examination
February/March, 2019

Marks Scored:

Level: B.E./B.Sc.
Year : II

Course : EEEG 202
Semester: I

Exam Roll No. : _____ Time: 30 mins.

F. M. : 20

Registration No.: _____

Date **FEB 22 2019**


SECTION "A"
[20 Q × 1 = 20 marks]

Encircle the most suitable answer to the following questions. Calculators are not allowed.

1. The output of a NOR gate is equivalent to _____.
- [a] NAND gate followed by an inverter [b] OR gate followed by an inverter
[c] AND gate followed by an inverter [d] NOR gate followed by an inverter

2. An active high OR gate is equivalent to active low _____.
- [a] AND gate [b] NOR gate [c] NAND gate [d] X-OR gate

 3. Implementing the expression $X = [A' B' + (C + D + E)]'$ with NOR logic, we get:



- [a] (A) [b] (B) [c] (C) [d] (D)

4. The function $F = ab + bc' + ac$ gives the same output as that of

- i) $ac + bc'$
ii) $(b+c)(a+c')$
iii) $(a'+c')(b'+c)$
iv) $(a+c)(b+c')$
- [a] i only [b] iii only [c] i and ii [d] i and iii

5. The expression $F = A' + B' + C'$ is equivalent to which single gate?

- [a] NAND [b] NOR [c] OR [d] AND

6. $(935)_{12}$ is equivalent to _____.

- [a] $(1337)_{10}$ [b] $(2470)_8$ [c] $(10111000110)_2$ [d] $(2480)_8$

7. _____ is represented by the following figure.
 [a] SR flip-flop with A = S and B = R [b] JK flip-flop with A = K and B = J
 [c] A JK flip-flop with A = J and B = K [d] SR flip-flop with A = R and B = S

 


Figure 1

8. The binary representation of BCD number 00101001 is _____.
 [a] 0011101 [b] 0110101 [c] 1101001 [d] 0101011
9. If $(100111001)_2$ is 2's complement number, it is equivalent in decimal as _____.
 [a] 199 [b] -199 [c] 313 [d] -313
10. If there are 52 unused states in a counter, it must be a _____.
 [a] 6 bit ring counter [b] 12 bit johnson counter
 [c] 12 bit ring counter [d] 6 bit twisted ring counter
11. Flip-Flops can be constructed with two _____.
 [a] XOR gates [b] NAND gates [c] AND gates [d] NOT gates
12. A mod-20 counter can ultimately _____.
 [a] divide the clock frequency by 20 [b] divide the clock frequency by 32
 [c] divide the clock frequency by 16 [d] multiply the clock frequency by 16
13. An eight bit serial in/serial out shift register is used with a clock frequency of 2 MHz to achieve a time delay of _____.
 [a] 4 μ sec [b] 2 μ sec [c] 0.5 μ sec [d] 1 μ sec
14. _____ chooses single line from multiple lines and directs the binary data to the output line.
 [a] Data selector [b] Data distributor [c] Decoder [d] Encoder
15. The initial state of MOD -16 down counter is 0110. After 37 clock pulses, the state of the counter will be _____.
 [a] 1011 [b] 0110 [c] 0101 [d] 0001

FEB 2 2 2019

16. The normal output of D latch _____.
- [a] follows the input when EN is low [b] complements the input when EN is high
[c] follows the input regardless of EN [d] follows the input when EN is high
17. Code is a symbolic representation of _____.
- [a] continuous signal [b] discrete signal
[c] binary information into decimal [d] decimal information into binary
18. The circuit shown in Figure 2 realizes the function _____.
- [a] $(A'+B')C+(DE)'$ [b] $A'+B'+C'+D'+E'$
[c] $AB+C(D+E)$ [d] $AB+C+DE$

 


Figure 2

19. Which of the following is not equivalent to X' ?
- [a] $X \text{ NAND } X$ [b] $X \text{ NOR } X$ [c] $X \text{ NAND } 1$ [d] $X \text{ NOR } 1$
20. The functional difference between SR and JK flip flop is _____.
- [a] JK flip-flop has a feedback path
[b] JK flip-flop requires no external clock
[c] JK flip flop is faster than SR flip flop
[d] JK flip flop can accept both inputs



KATHMANDU UNIVERSITY
End Semester Examination
February/March, 2019

FEB 22 2019

Level : B.E./B.Sc.
Year : II
Time : 2 hrs. 30 mins.

Course : EEEG 202
Semester: I
F. M. : 55

SECTION "B"

[5Q × 11 = 55 marks]

Attempt *ANY FIVE* questions.

1. a. What do you mean by self-complementing codes? Explain with suitable examples. [2]
b. Perform the following operations using 2's complement. Explain whether there is overflow in each case. [5]
 - i. Subtract $(-50)_{10}$ from $(+100)_{10}$
 - ii. Add $(-85)_{10}$ to $(-97)_{10}$
- c. Define timing diagram for combinational logic gates? Explain three input NOR gate with timing diagram. [4]
2. a. Find (r-1)'s complement of $(1001.001)_2$ and $(27.95)_{10}$. [2]
b. Construct an 8×1 multiplexer using 2×1 multiplexer. [4]
c. Design a combinational logic circuit with 4 inputs and 4 outputs that converts a 4 bit gray code into equivalent excess-3 code. [5]
3. a. Design a BCD adder. [5]
b. Implement following functions using decoder. [4]
$$F1 = (A+B'+C) (B+C+D')$$
$$F2 = (A+B+C') (A+D)$$

c. Explain the significance of priority encoder. [2]
4. a. Differentiate between characteristic table and excitation table? Obtain the characteristic table and characteristic equation for negative edge triggered S'R' flip flop. [1+4]
b. Design a 4 bit synchronous up counter which displays even decimal number in binary format. [6]
5. a. Compare counters and registers. Design a mod -12 asynchronous down counter. [2+4]
b. Explain how a universal register can be used as different types of registers. [5]
6. a. Design a sequential logic circuit that has 2 D flip flops and 2 inputs A and B. If $A = 0$, the circuit remains in the same state regardless the value of B. When $A = 1$ and $B = 1$, the circuit goes through the state transitions from 00 to 01 to 10 to 11 back to 00 and repeats. When $A = 1$ and $B = 0$, the circuit goes through the state transitions from 00 to 11 to 10 to 01 back to 00 and repeats. [5]
b. Write short notes on the following. [2+2+2]
 - i. Weighted binary code
 - ii. Applications of shift register
 - iii. Programmable logic array

